

Binary Multiplication

	A_2	A_1	A_0	Multiplicand
\times	B_2	B_1	B_0	Multiplier
	A_2B_0	A_1B_0	A_0B_0	
+	A_2B_1	A_1B_1	A_0B_1	\times
+	A_2B_2	A_1B_2	A_0B_2	$\times \quad \times$

- Combinational circuit Multiplier

Array Multiplier : because it consists of the array of the adders as well as the AND gates.



Then we will use the adders circuit to get final output.

N-bit Multiplication :

we need : N^2 - AND gates

N - Half adders

$N(N-2)$ - Full adders

→ For N-bit multiplier, if we consider:

T_A	=	T_C	=	T_S	=	1 unit delay
(AND gate)		(carry)		(sum)		

then to get the valid product output ,
 required delay \sim 2N unit delay

→ As N increases,

Required Hardware resources } increase
 Hence power consumption

⇒ Array Multipliers are not preferable for large value of N.

Signed binary Multiplication :

2's
complement
Form

Ex. 1

$$\begin{array}{rcl}
 -5 & \longrightarrow & 1011 \\
 \times 7 & \longrightarrow & 0111 \\
 \hline
 -35 & &
 \end{array}$$

2's complement

} ↑

Positive

n bits
 \times n bits

 2n bits

So now,

$$\begin{array}{r}
 1011 \\
 \times 0111 \\
 \hline
 1111\textcircled{1}011 \\
 111\textcircled{1}011 \times + \\
 11\textcircled{1}01 \times \times + \\
 0\textcircled{0}00 \times \times \times + \\
 \hline
 11011101 \longrightarrow \textcircled{-35}
 \end{array}$$

Ignore the extra
 MSBs in the
 answer.

Ex. 2

$$\begin{array}{rcl}
 -5 & \longrightarrow & 1011 \\
 \hline
 & &
 \end{array}$$

} 2's complement

$$\begin{array}{r} x \quad (- \quad +) \\ \hline 85 \end{array} \rightarrow \begin{array}{c} 1001 \\ \boxed{\text{Negative}} \end{array}$$

When multiplier is negative, we have to take 2's complement of last row to get the correct answer.

So now,

				1	0	1	1	
				1	0	0	1	
x				1	0	0	1	
1	1	1	1	1	0	1	1	
0	0	0	0	0	0	0	0	f
0	0	0	0	0	0	0	0	+
1	1	0	1	1	x	x	x	-
0	0	1	0	1	x	x	x	+
1	0	0	1	0	0	0	1	1

ignore this bit

35

important for -ve Multiplier

take 2's complement & add to the answer

Note : now, since this is signed multiplication, if we apply this rule to the positive multiplier also, it won't change anything.
 → cause, signed +ve multiplier

⇒ M.S.B. "0" ⇒ Partial products "0...0" All zeroes

taking 2's complement won't affect anything since we are ignoring

case we are ignoring
the extra bits.